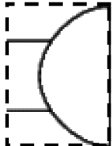
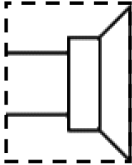
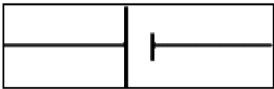


I2








Steady Hand Game

Electrical Components

	Buzzer
	Loudspeaker
	Lamp
	Switch
	Cell
	Heater
	Motor
	Switch

I2


Steady Hand Game

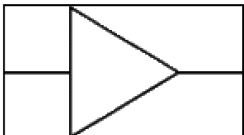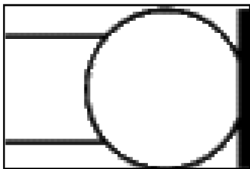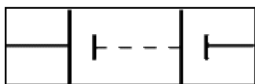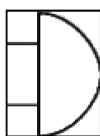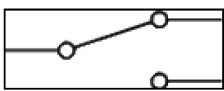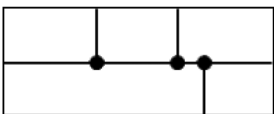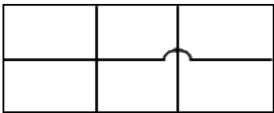	Amplifier
	Microphone
	LED
	Battery
	Bell
	2– Way Switch
	Wires Joined
	Wires Not Joined

I2

Steady Hand Game

Steady Hand Diagram

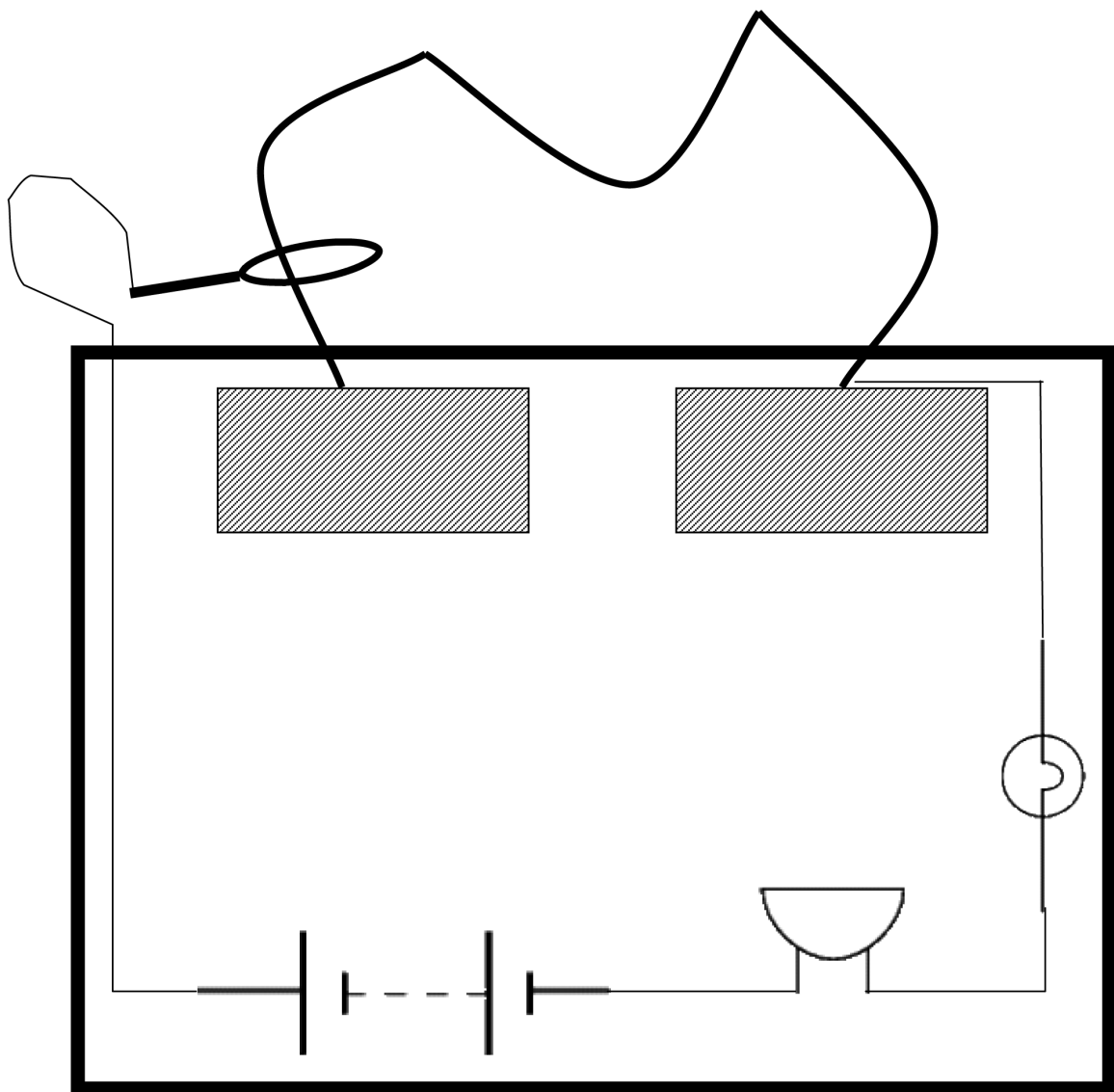

Battery Tester Template

